

2015

# SIMPLE TWO SENSOR BASED LINE FOLLOWER ROBOT WITHOUT MICROCONTROLLER

Riddha Manna  
B. Tech  
NIT Durgapur



## Introduction

In this tutorial, we'll make a simple line follower which follows a black line on a white or vice-versa using simple basic components.

### Things required

1. Sensor pairs (either LED-LDR or IR LED-Photodiode) (2)
2. 10k Ohm Potentiometers (2)
3. 7805 voltage regulator.
4. LM339 comparator IC (1)
5. L293D motor driver IC (1)
6. 74LS04 Not Gate (1)
9. Breadboard (1)
10. A differential drive chasis

### Sensor Circuit

We'll be basically dealing with two circuits here.

i) Sensor Circuit


ii) Comparator-bjt circuit

Sensor Circuit

The sensor circuit will basically tell you whether your robot is on the line or out of line. The sensors suitable for this purpose are LED-LDR sensor, or IR LED-Photodiode sensor pair.

Now, let us see how it'll help to differentiate the line from the surface. We know the fact that a white surface will anytime reflect more rays than a black surface. This is the basic principle that we use to judge whether the sensor pair is on white line or black line.

Consider this LED-LDR sensor pair.

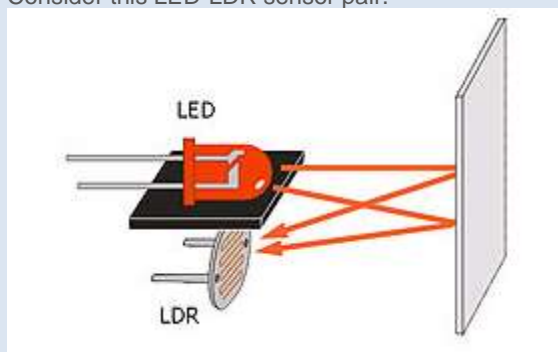

Now, when this sensor pair is on a white line,

=> more led light reflected by the surface

=> more light falls on LDR

=> lesser LDR resistance

=> the voltage across LDR will be less


Similarly, when the sensor pair is on a black line,

=> the voltage across LDR will be high.

The 10k component is your potentiometer which you might have to set to the maximum range. This resistance, ideally should be near  $(R(\text{light}) * R(\text{dark}))^{1/2}$  where,  $R(\text{light})$  is the approximate resistance of LDR during light and  $R(\text{dark})$  is the resistance of the same in dark.
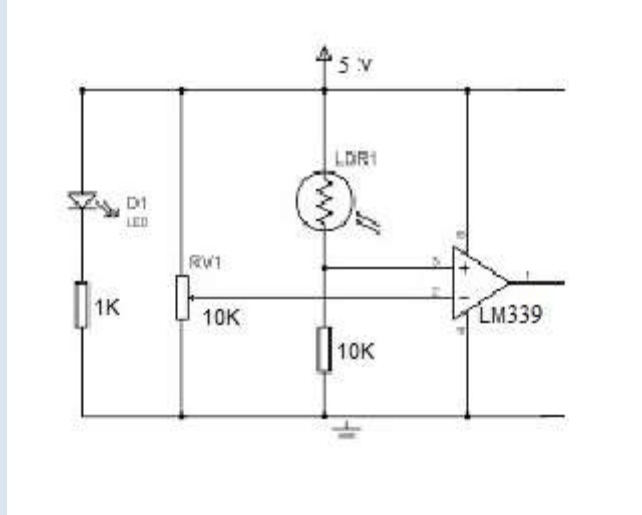
### Comparator Circuit

Now for analysing the sensor output, we use a comparator to get a digital output.



Now, the LED-LDR is connected to a comparator LM339. LM339 is an operational amplifier IC which is being used as a comparator. The non inverting terminal of op-amp (The + terminal) reads the voltage across resistor R. And, the inverting terminal of op-amp (The – terminal) reads the voltage that has been set at the potentiometer.

When on white line,  $V(\text{ldr})$  less  $\Rightarrow V_{\text{out}}$  more.

When on black line,  $V(\text{ldr})$  more  $\Rightarrow V_{\text{out}}$  less.

The voltage of at potentiometer (- terminal),  $V(\text{pot})$  is such that :

$$V_{\text{white}} > V(\text{pot}) > V_{\text{black}}$$

Such a voltage is set by setting up the corresponding potentiometer resistance.

Hence, now

When sensor on white line :

$$V_{\text{white}} > V(\text{pot})$$

$$\Rightarrow V_+ > V_-$$

$$\Rightarrow \text{Op-amp output} = \text{High}$$

When sensor on black line :

$$V(\text{pot}) > V_{\text{black}}$$

$$\Rightarrow V_- > V_+$$


$$\Rightarrow \text{Op-amp output} = \text{Low}$$

This is how we know whether the sensor is on black or white line.
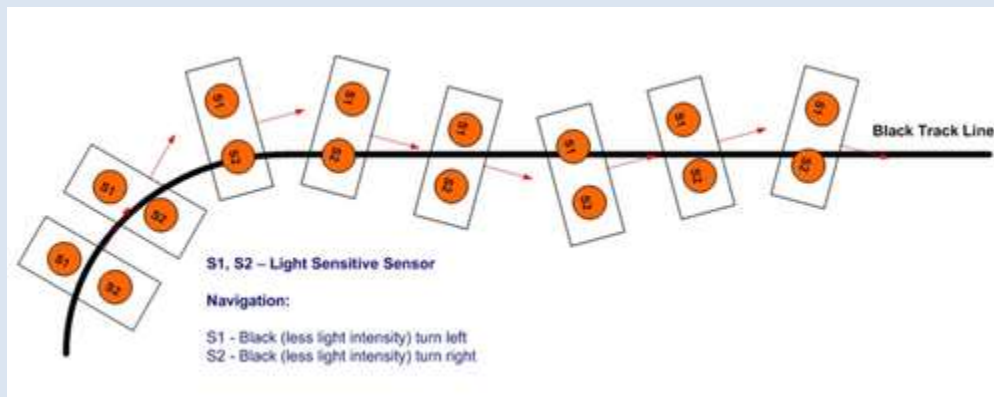
### Algorithm

Now, how do we implement this on our line follower?

In this tutorial, we'll be making a 2 sensor line follower which will be working as –



For the turns, we have two motors running in opposite directions.

### Final Circuit

